

# UC20&M10 Reference Design Explanation

## 1. The difference on the interface between UC20 and M10.

Refer to the document <UC20&M10\_Compatibility\_Design> for more details.

## 2. The explanation of compliant footprint.

Refer to the document <UC20\_Hardware\_Design> and our reference footprint for more details.

## 3. The difference on the voltage level between UC20 and M10.

	VBAT	VDD_EXT	VRTC	PWRKEY	RESET_N/EMERG_OFF	NET_STATUS/NETLIGHT	ADC	UART	ANT_MAIN
UC20	3.4~4.3	1.8	1.5~3.2	1.8	1.8	1.8	0.2~2.1	1.8	GSM+WCDMA
M10	3.3~4.6	2.8	1.5~3.3	VBAT	2.8	2.8	0~2.8	2.8	GSM Quad-band

## 4. The explanation of compliant circuit.

Refer to the related sheet for details.

## 5. Index of reference design.

Sheet 1: Design Explanation

Sheet 2: Module Interface

Sheet 3: Power Supply Design

Sheet 4: UART and SIM Design

Sheet 5: Audio Design

Sheet 6: RF and GPS Design


Sheet 7: Other Designs

Sheet 8: MCU Interface

Quectel Wireless Solutions

DRAWN BY <Mountain.ZHOU>	PROJECT <UC20&M10 Reference Design>	TITLE <Design Explanation>
CHECKED BY <Bruce.YU>	SIZE A2	VER 1.01
SHEET 1 of 8	<2013.04>	

# Module Interface

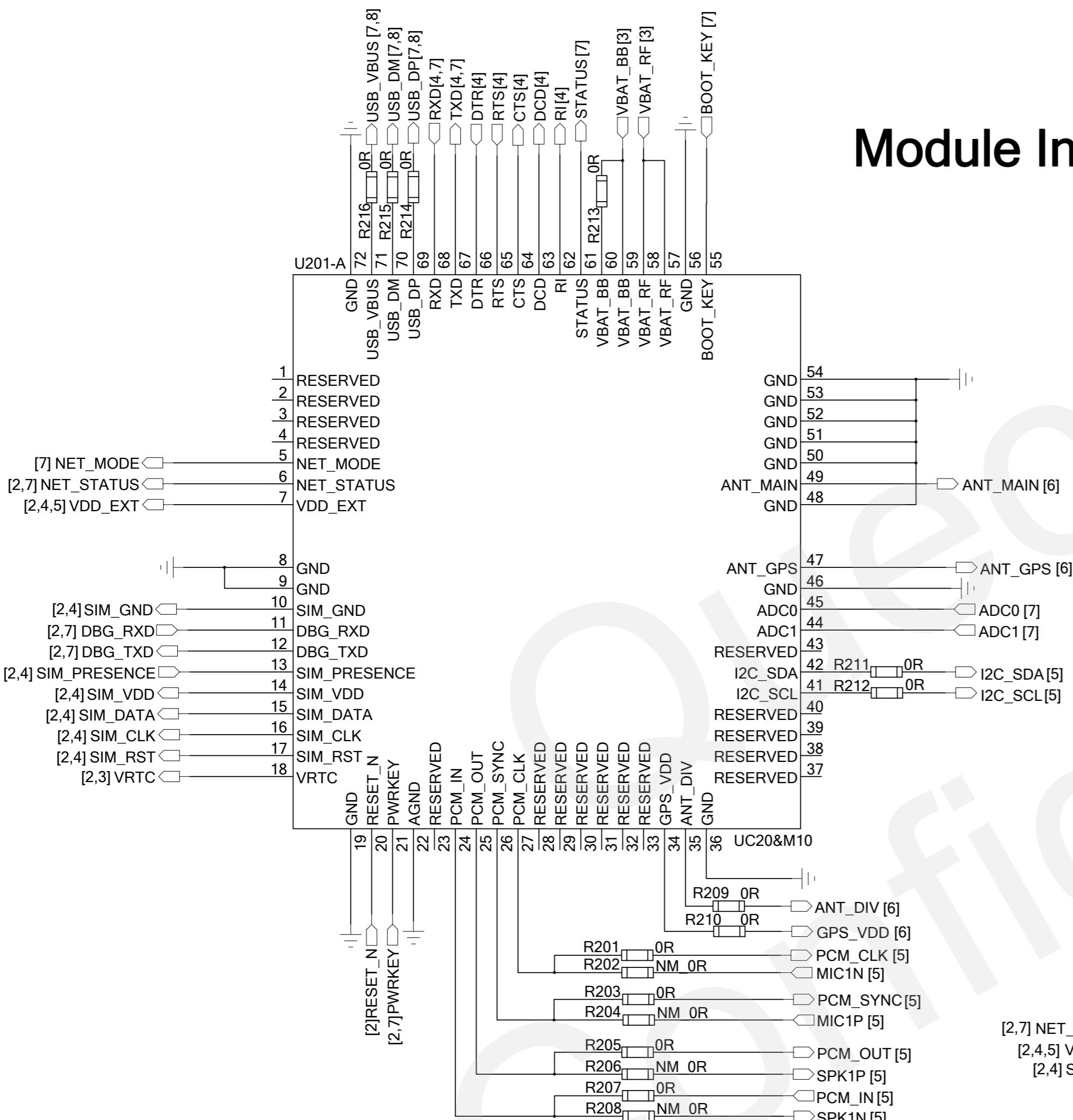

When M10 is applied, SIM\_GND connects to M10 GND pin.



Notes:

1.The SMD difference between UC20 and M10.



Intended audience	Installed	Not installed
M10	R202, R204, R206, R208	R201, R203, R205, R207, R209~R216
UC20	R201, R203, R205, R207, R209~R216	R202, R204, R206, R208

2.Please refer to sheet 1 and M10 and UC20 Hardware Design respectively for further details about the difference between them.

3.Keep all reserved pins open.

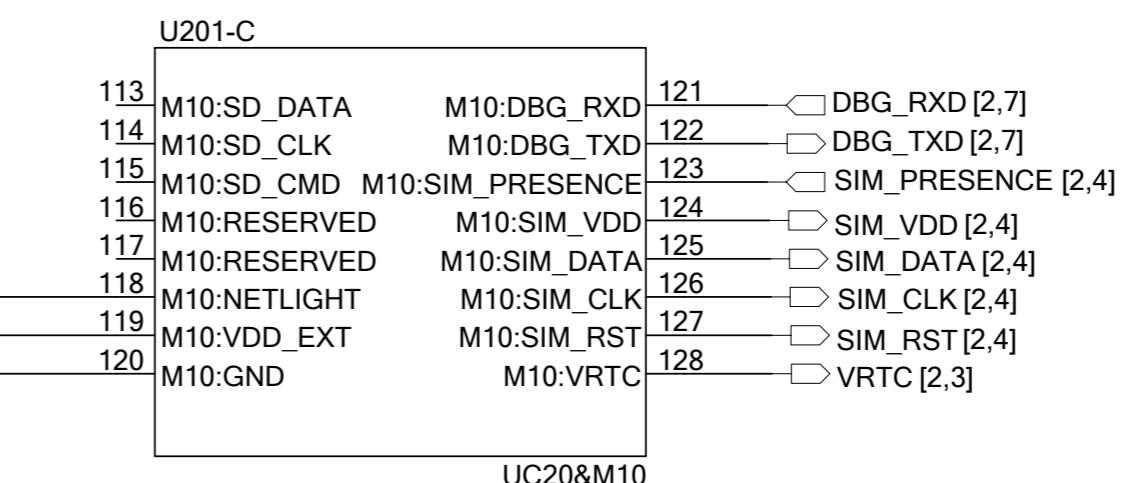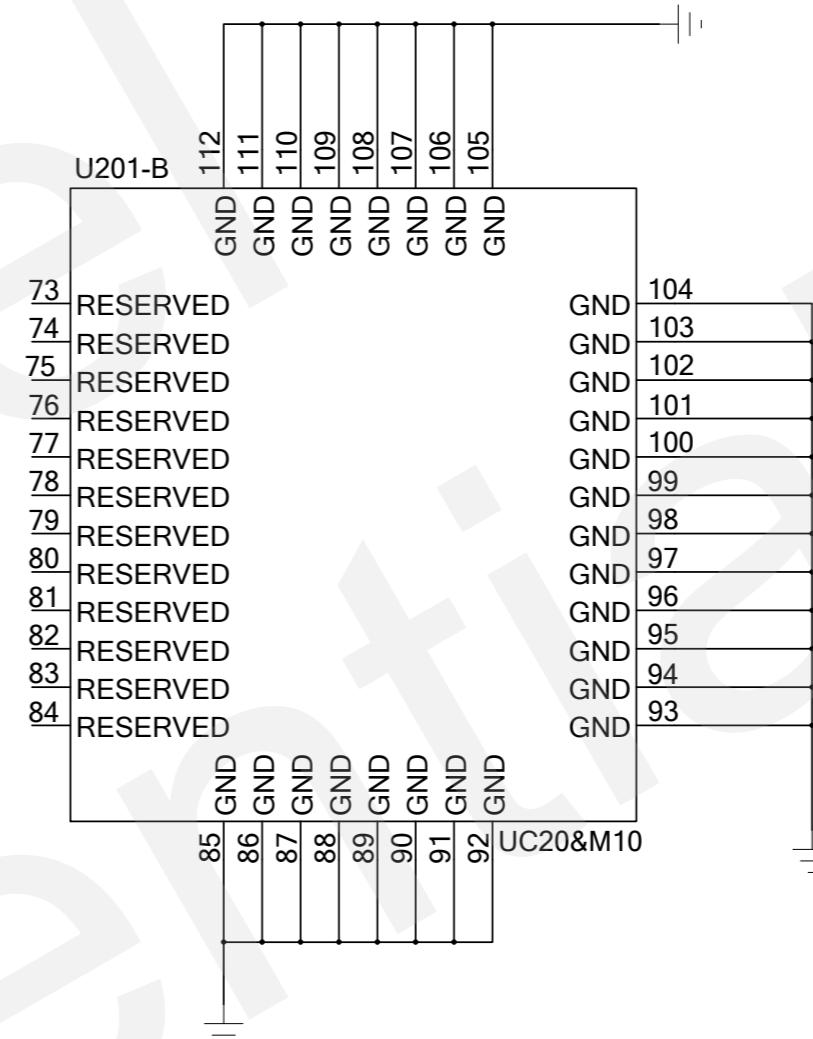

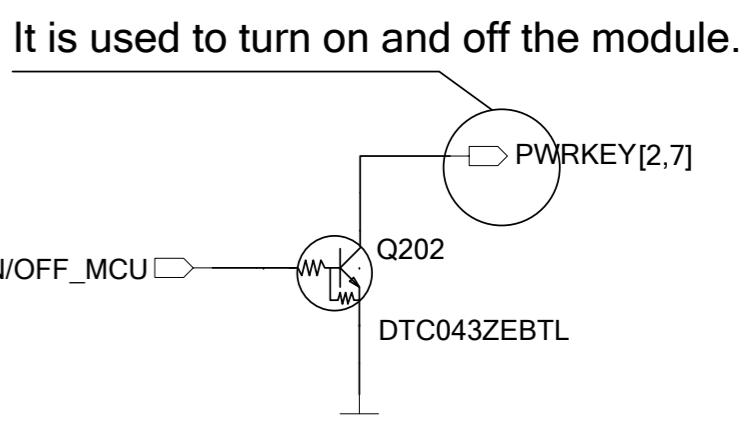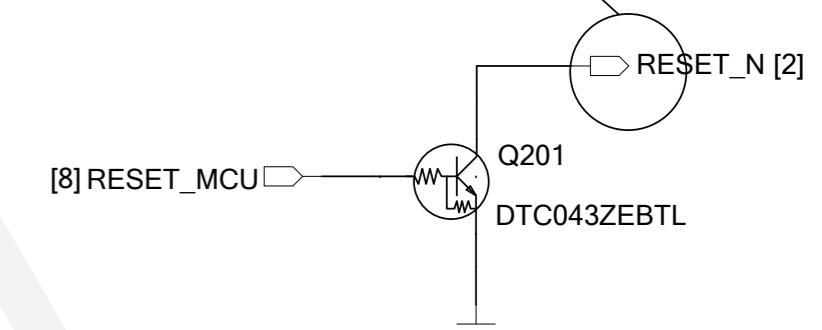For UC20, it is used to reset the module.  
For M10, it is EMERG\_OFF used to turn off the module.




## Quectel Wireless Solutions

DRAWN BY <Mountain.ZHOU>	PROJECT <UC20&M10 Reference Design>	TITLE <Module Interface>
CHECKED BY <Bruce.YU>	SIZE A2	VER 1.01
SHEET 2 of 8		<2013.04>


# Power Supply Design
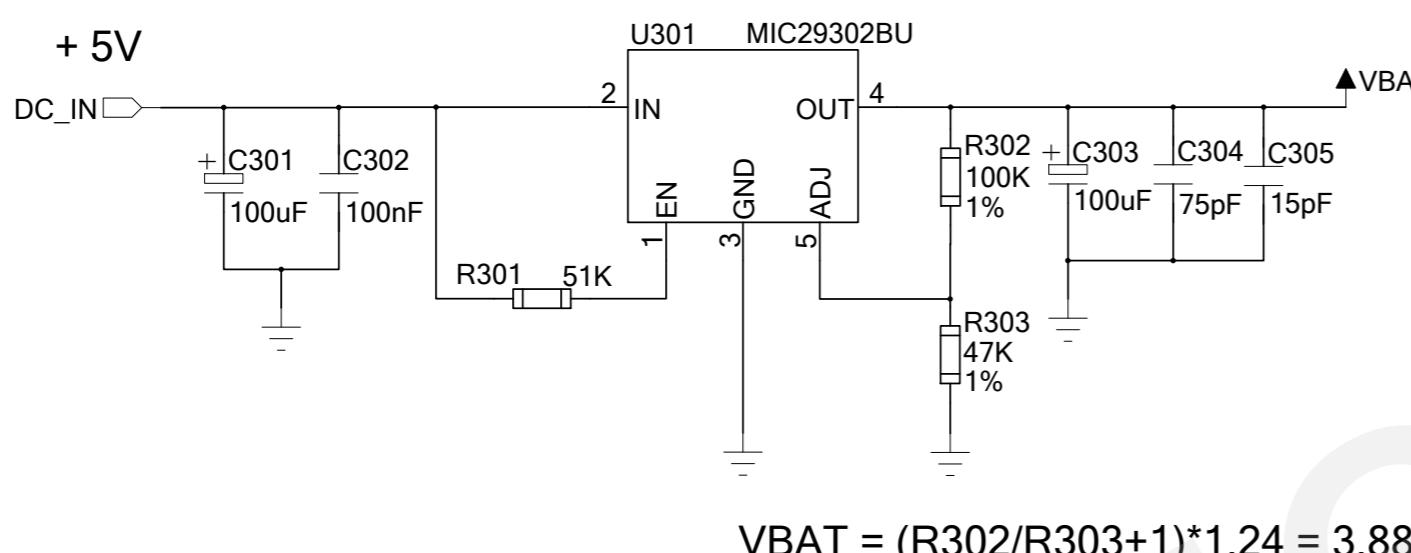
## LDO Application

It is used when the input voltage is below 7V.



## VRTC Design

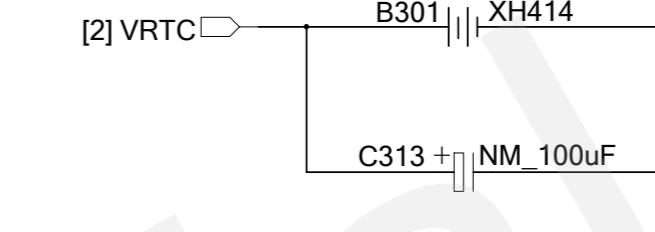


## DC-DC Application


1. It is used when the input voltage is above 9V in the vehicle application.

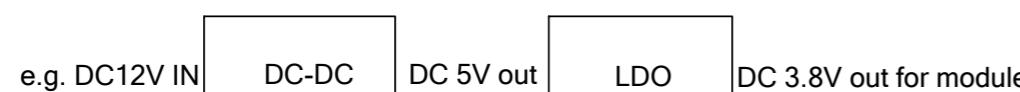2. Use DC-DC to convert high input voltage to 5V,


and LDO will generate 3.8V typical voltage for the module.



## VBAT Design

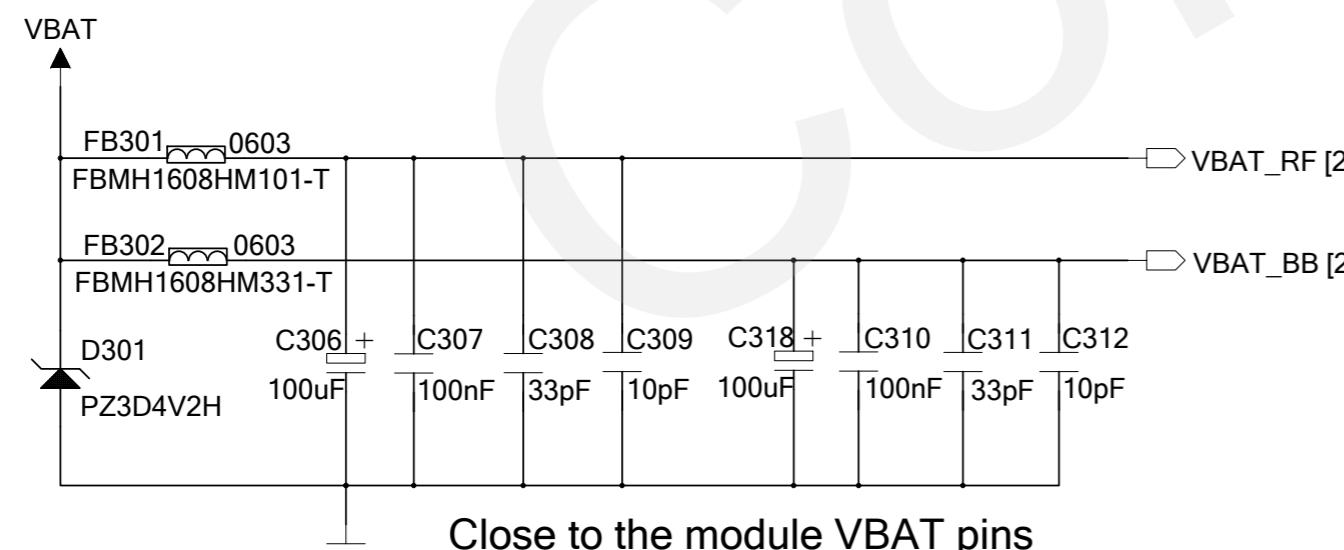

## Power for PCM Codec and ADC Circuit

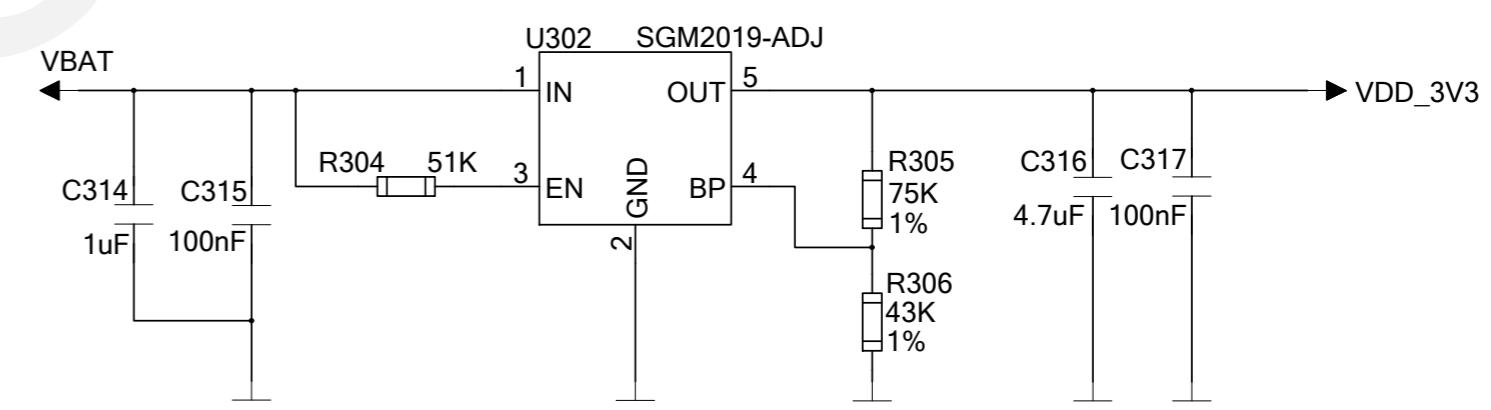


Quectel Wireless Solutions

DRAWN BY <Mountain.ZHOU>	PROJECT <UC20&M10 Reference Design>	TITLE <Power Supply Design>
CHECKED BY <Bruce.YU>	SIZE A2	VER 1.01
SHEET	3 of 8	<2013.04>

# UART and SIM Design

## UART Level Translator

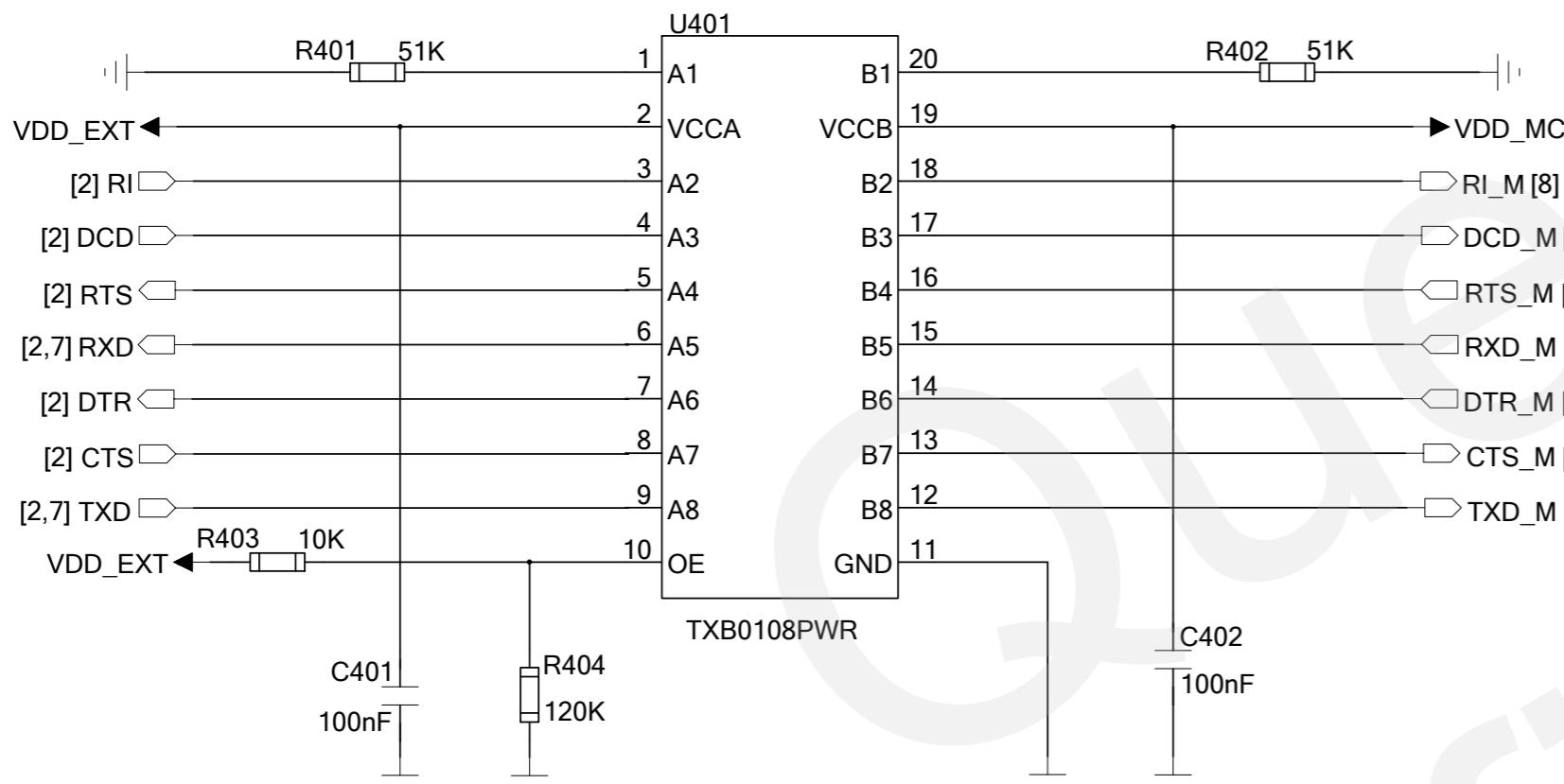


### Notes:

- 1.TXB0108 is to realise the voltage level translation between UC20/M10 and MCU.
- 2.This circuit is available for both UC20 and M10 UART voltage level translation design.
- 3.VCCA should not exceed VCCB.

For more information about TXB0108, please refer to the datasheet.

## SIM Design

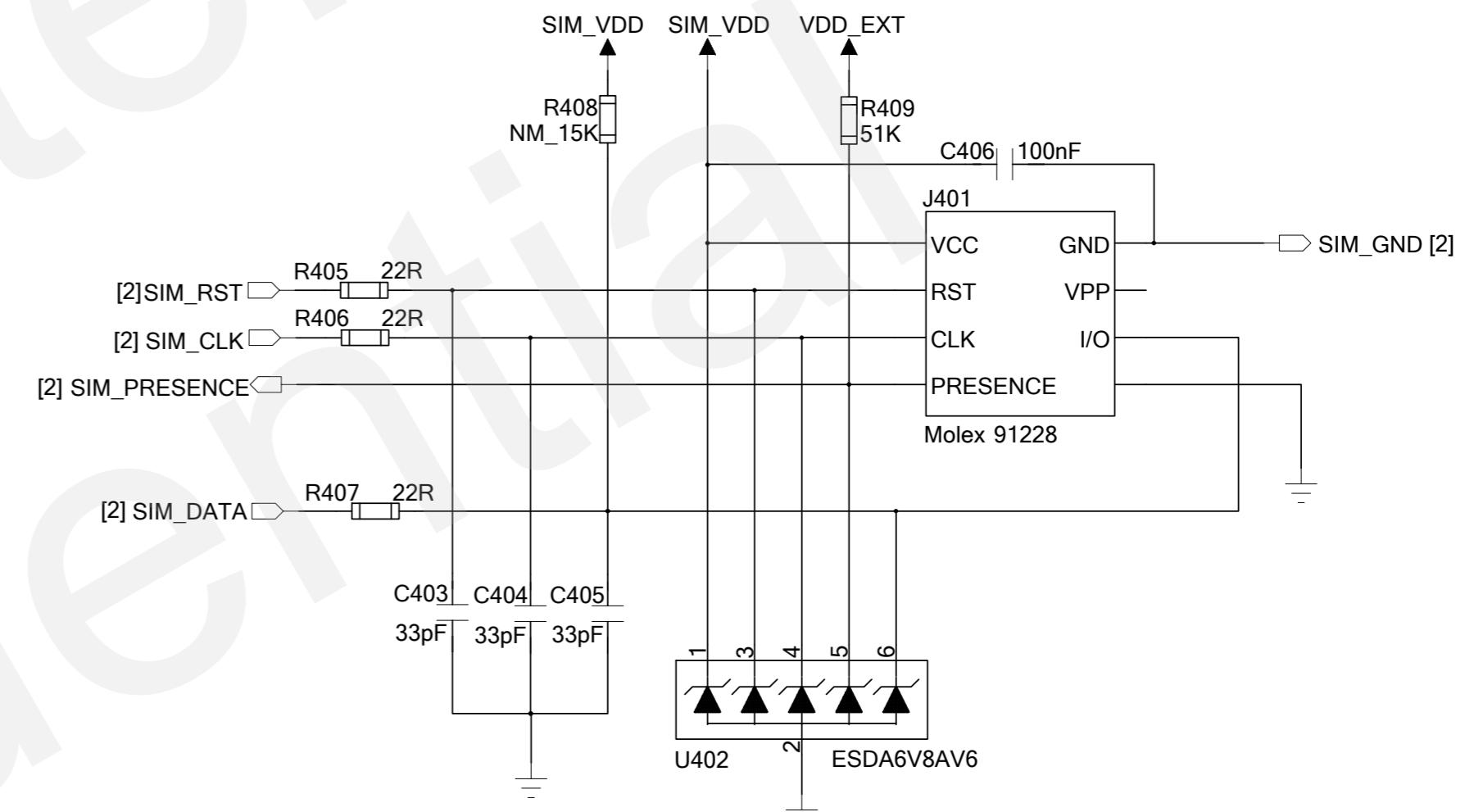

### Notes:


- 1.R405~R407 are applied to suppress the EMI spurious transmission and enhance the ESD protection.
- 2.R408 is reserved to improve anti-jamming capability for long SIM\_DATA layout trace.
- 3.SIM\_PRESENCE is used to detect SIM card, which will be low when the SIM card is inserted. This function on UC20 is not supported currently.
- 4.The value of C406 should be less than 1uF.

## Quectel Wireless Solutions


DRAWN BY <Mountain.ZHOU>	PROJECT <UC20&M10 Reference Design>	TITLE <UART and SIM Design>
CHECKED BY <Bruce.YU>	SIZE A2	VER 1.01
SHEET 4 of 8		<2013.04>

# Audio Design


## PCM Codec Circuit

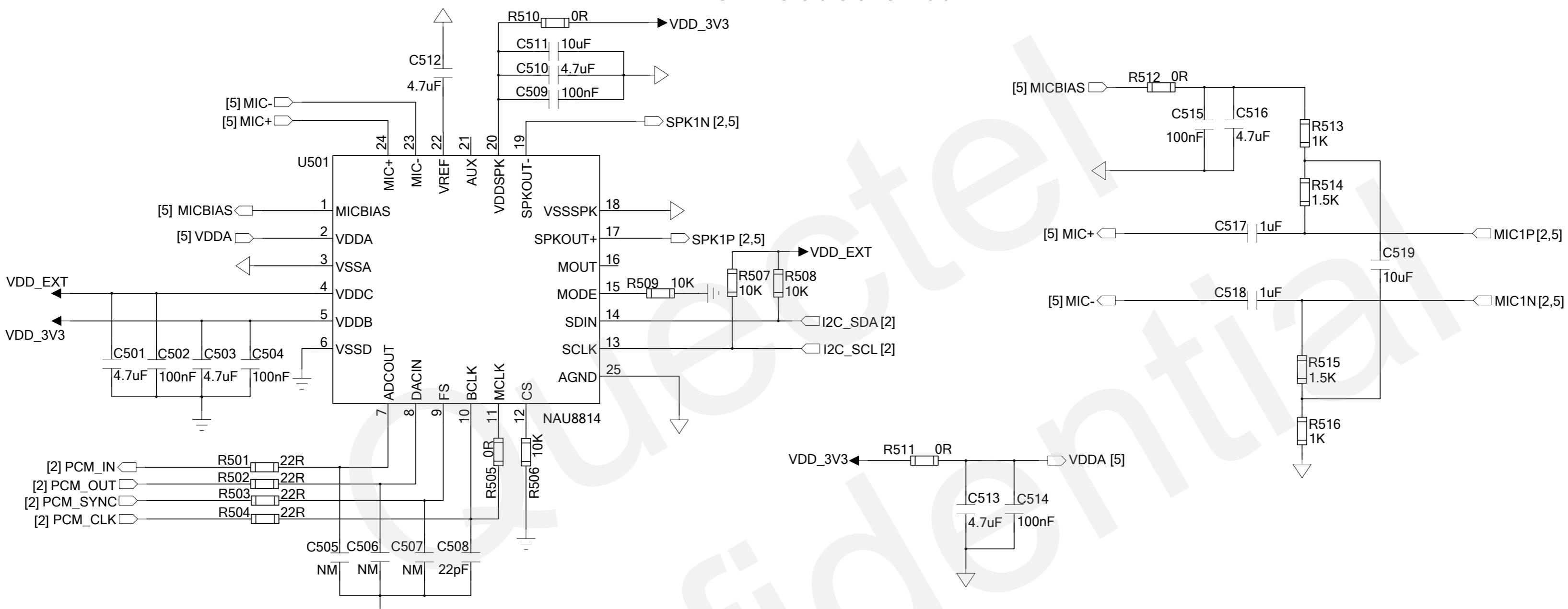

## Audio Channel - Earphone

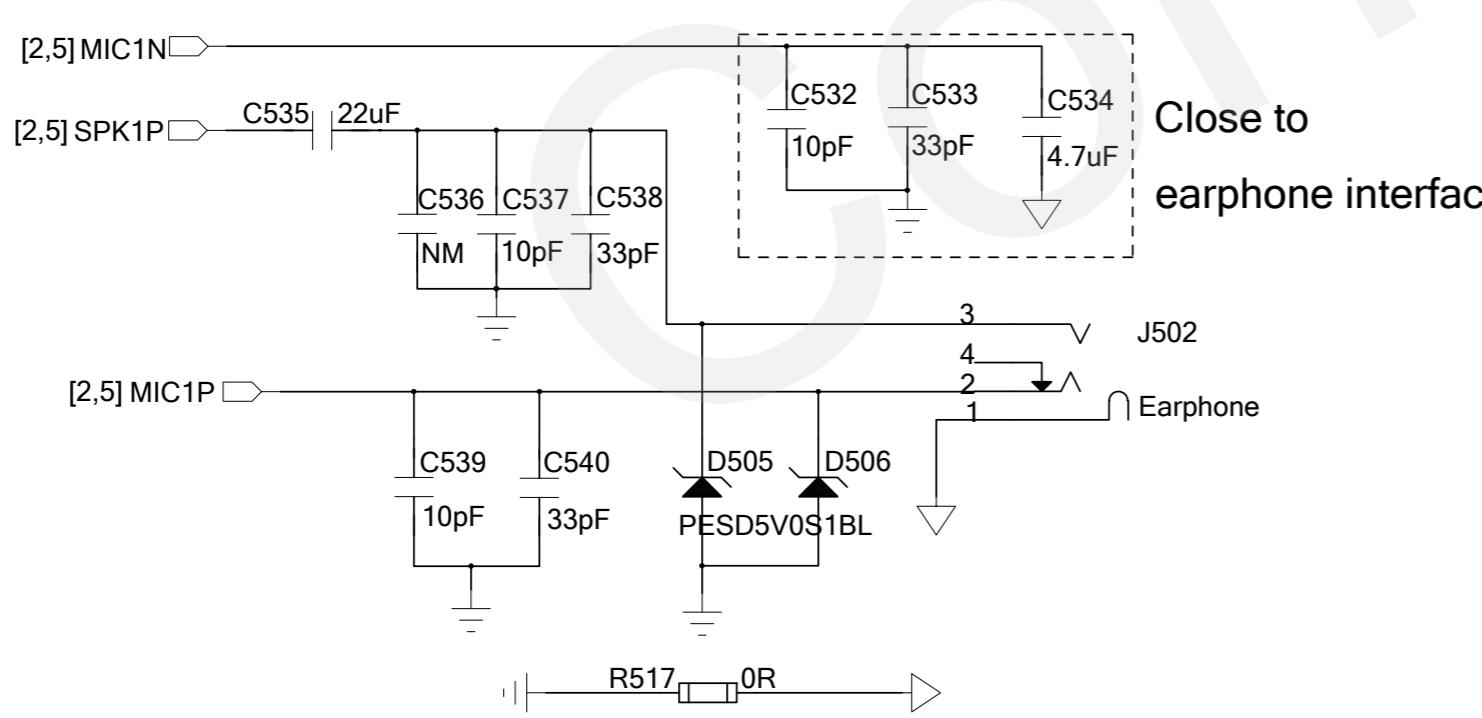

## Audio Channel - Handset

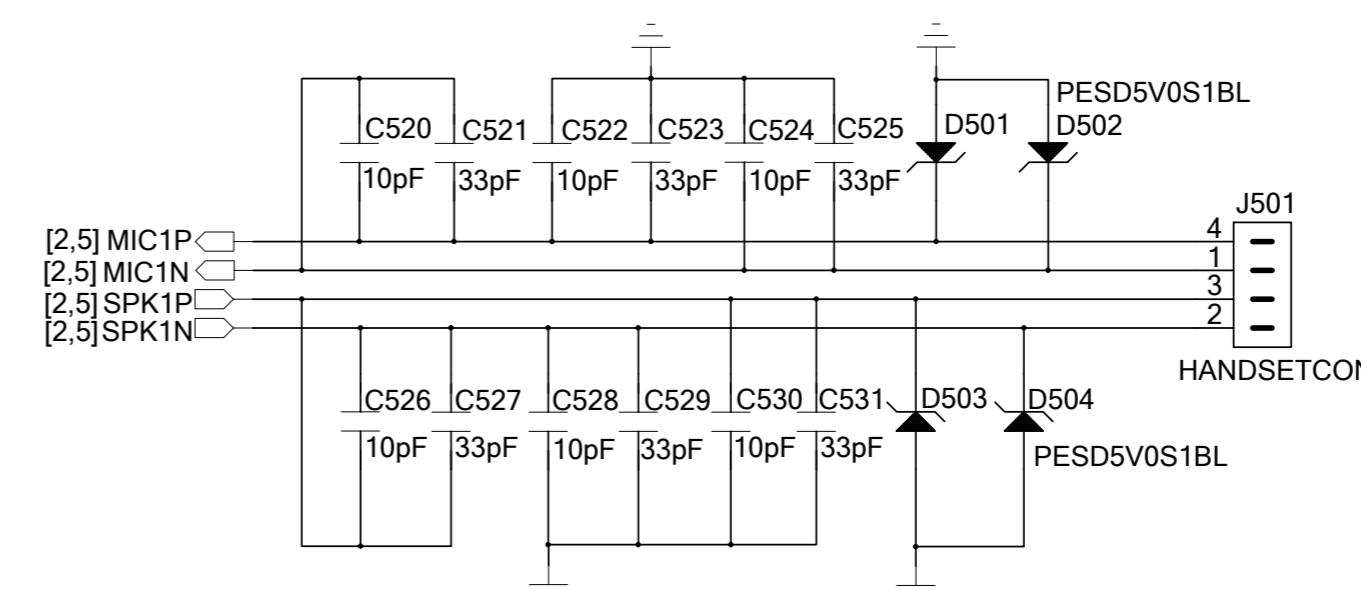


### Quectel Wireless Solutions


DRAWN BY <Mountain.ZHOU>	PROJECT <UC20&M10 Reference Design>	TITLE <Audio Design>
CHECKED BY <Bruce.YU>	SIZE A2	VER 1.01
SHEET 5 of 8	<2013.04>	

# RF and GPS Design

## Main Antenna Interface


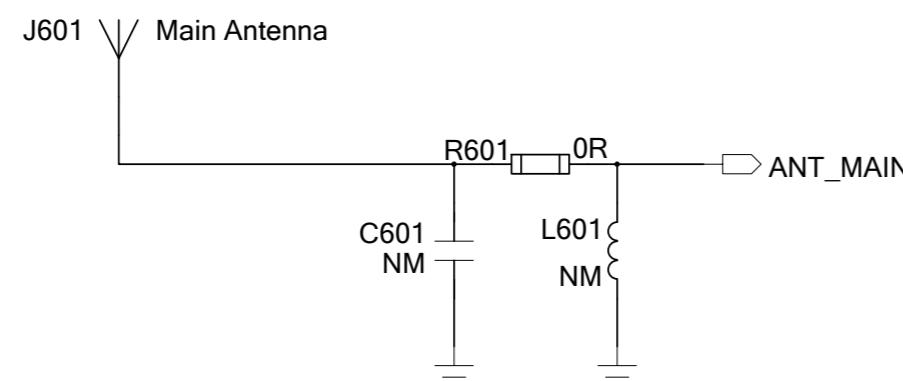


## Diversity Antenna Interface

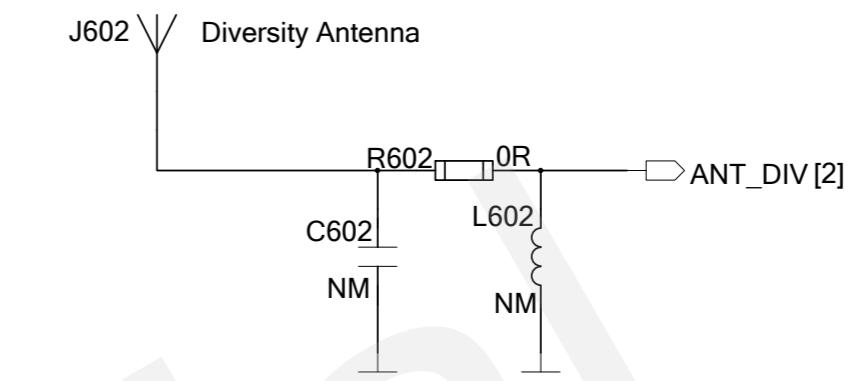

ANT\_DIV is used to improve RF signal reliability and quality.

## GPS LNA Circuit

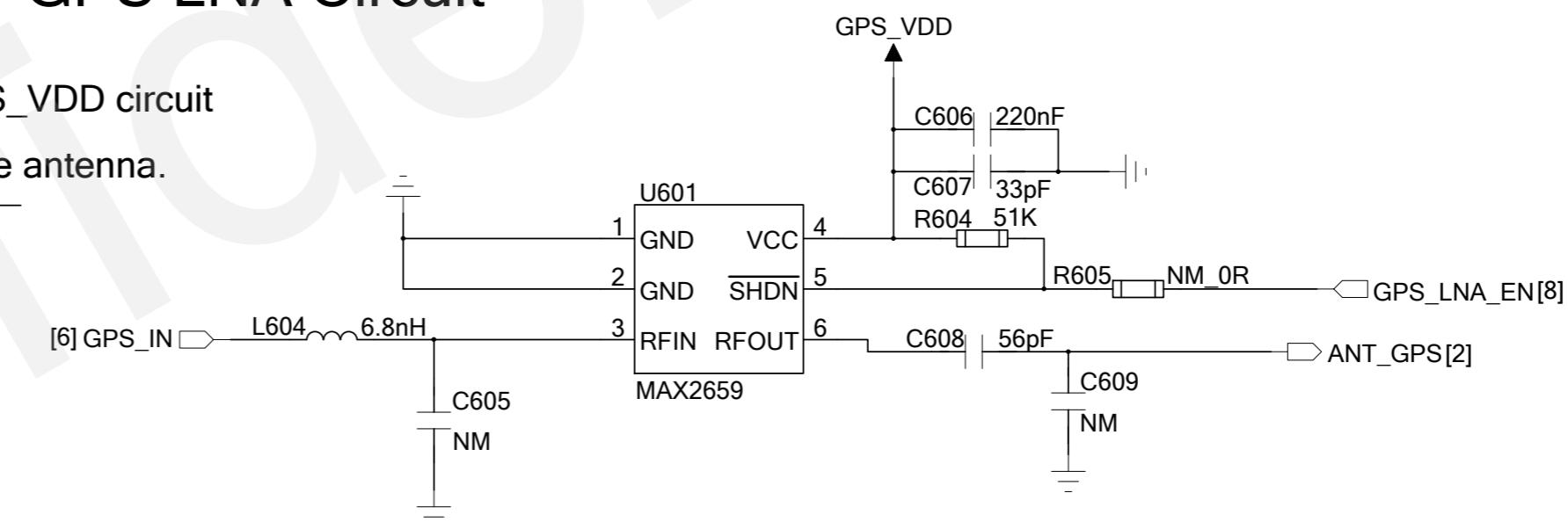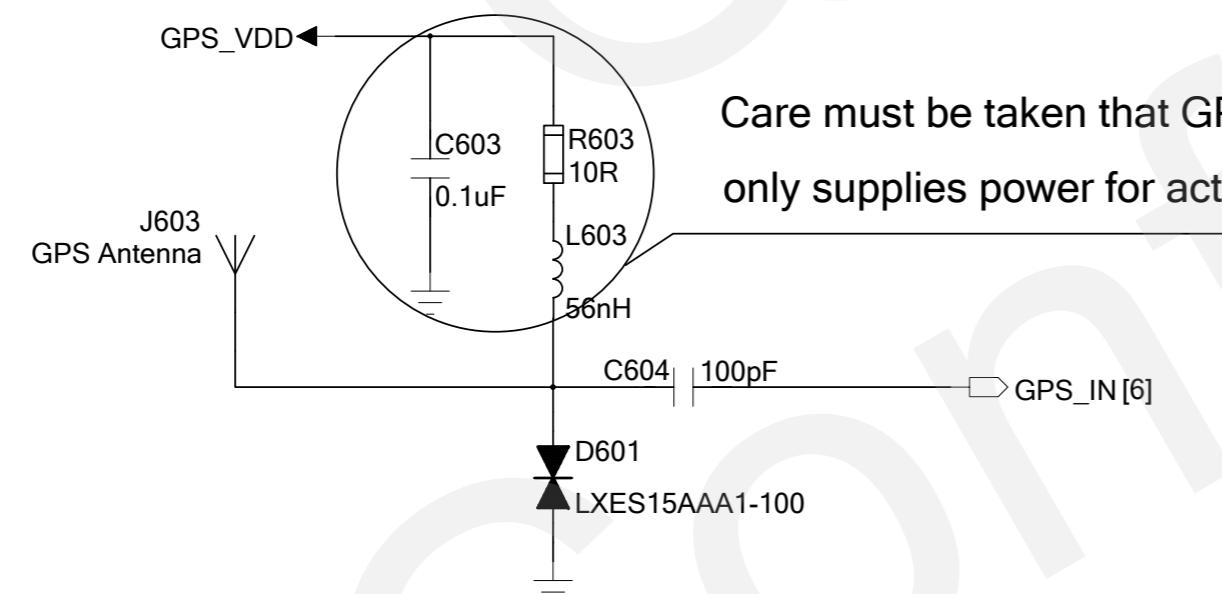


### Notes:

- 1.R603 is designed with GPS antenna short-circuit protection function, which can prevent module from being damaged. The rated power of R603 should be up to 1W.
- 2.The GNSS-capable antenna is needed to support both GPS and GLONASS system in the future.
- 3.Customer can use one GPIO to turn on and off the LNA U601 to save the power.
- 4.The GNSS-capable front-end LNA is needed to support both GPS and GLONASS system in the future.

### Quectel Wireless Solutions



DRAWN BY <Mountain.ZHOU>	PROJECT <UC20&M10 Reference Design>	TITLE <RF and GPS Design>
CHECKED BY <Bruce.YU>	SIZE A2	VER 1.01
SHEET 6 of 8		<2013.04>

# Other Designs

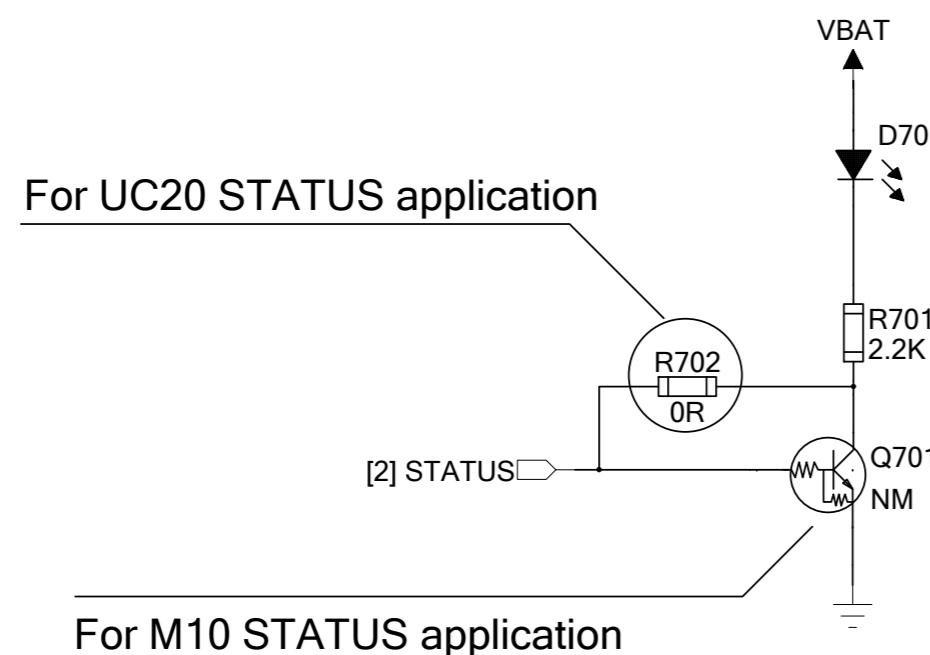

For M10 STATUS application

## Indicator

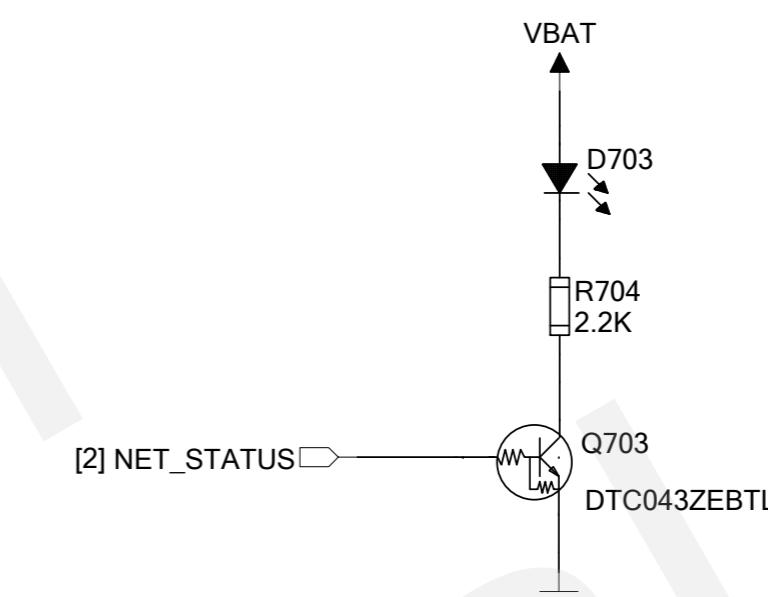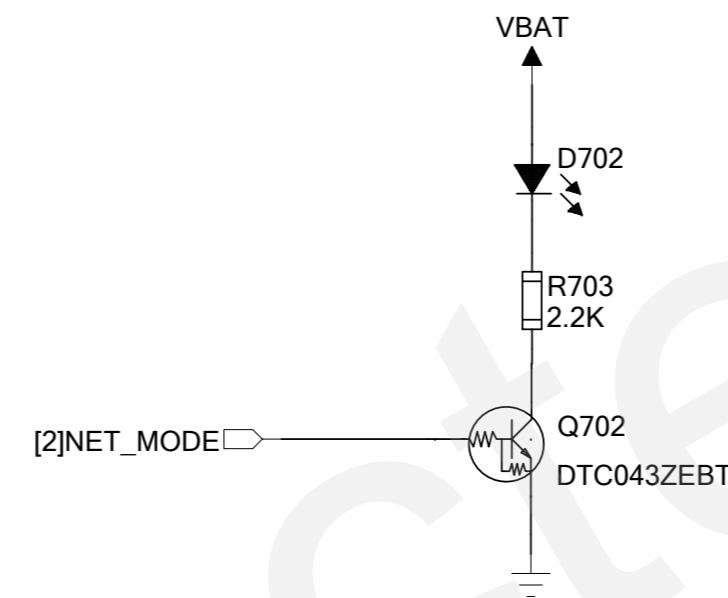

Note:

Refer to the document <UC20\_Hardware\_Design> for more details about NET\_MODE and NET\_STATUS.



## Reserved Testpoints

U701	
1	VBAT [3,7]
2	
3	PWRKEY [2]
4	BOOT_KEY [2]
5	USB_VBUS [2,8]
6	USB_DM [2,8]
7	USB_DP [2,8]
8	TXD [2,4]
9	RXD [2,4]
10	DBG_TXD [2]
11	DBG_RXD [2]

Notes:

1. USB and BOOT\_KEY pins are used to upgrade UC20 firmware.  
BOOT\_KEY needs to be pulled high before upgrading, and keep open in normal mode.  
Refer to the document <UC20\_Hardware\_Design> for more details about BOOT\_KEY.
2. M10 upgrades firmware via main UART port (TXD/RXD).
3. Debug UART pins can only be used to catch log.
4. It is recommended to add ESD protection components (e.g. ESDA6V8AV6) on these reserved testpoints. In addition, the ESD diodes used on USB data lines should have less than 2 pF of capacitance.

## ADC Design

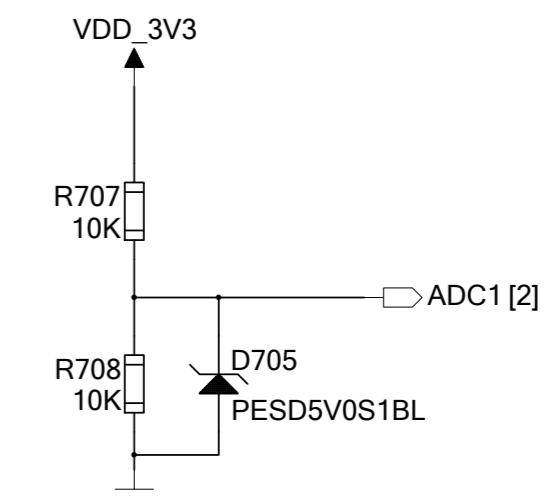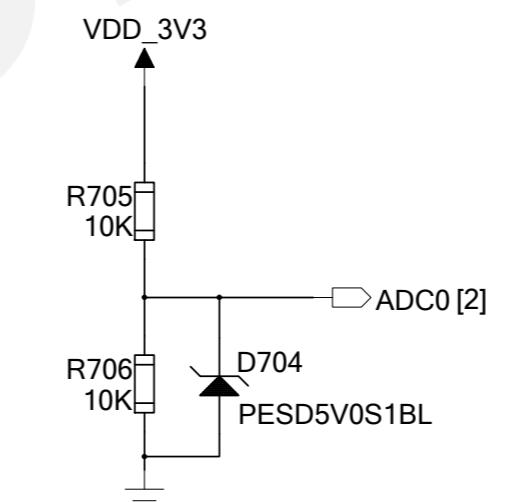



Note:

Input voltage range of UC20 and M10 ADC channels is 0.2~2.1V and 0~2.8V respectively.

## Quectel Wireless Solutions

DRAWN BY <Mountain.ZHOU>	PROJECT <UC20&M10 Reference Design>	TITLE <Other Designs>
CHECKED BY <Bruce.YU>	SIZE A2	VER 1.01
	SHEET 7 of 8	<2013.04>

# MCU Interface

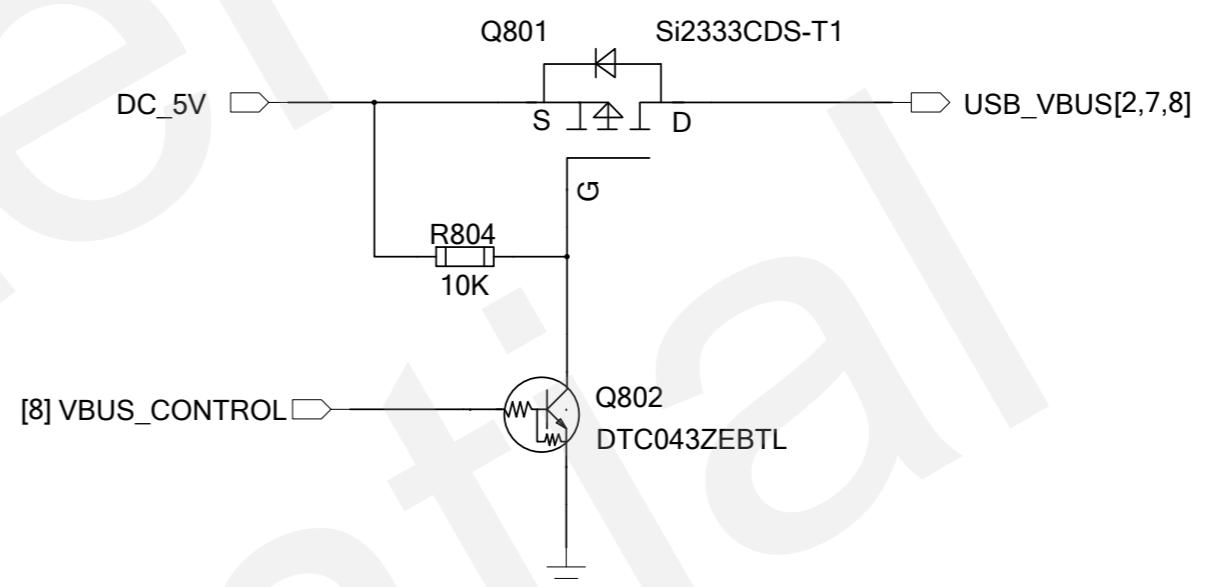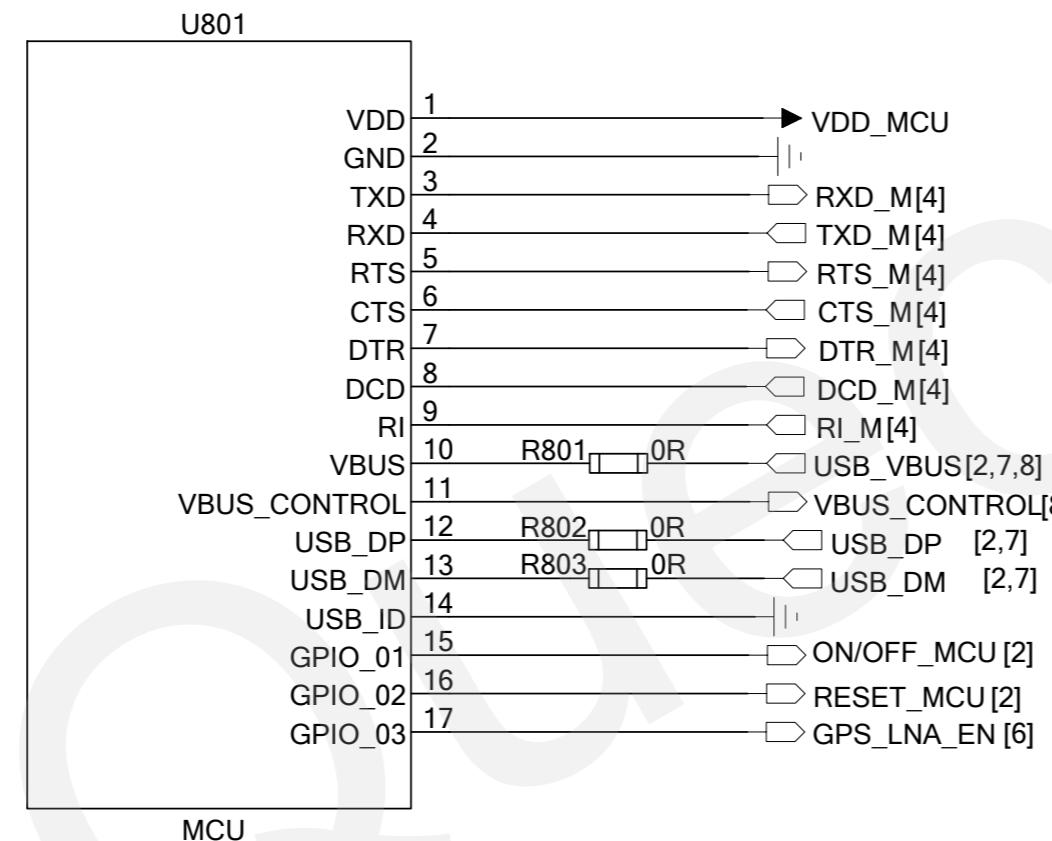

VBUS\_CONTROL = High level, Q801 conducts.

## Notes:

- 1.U801 represents customer's MCU.
- 2.Pay attention to the UART connection of RTS/CTS.
- 3.UC20 can only work as a USB device and supports LS/FS/HS mode. To communicate with USB interface, MCU needs to support USB host or OTG function.  
The VBUS pin of MCU and UC20 need to be provided 5V power for detection, and VBUS\_CONTROL turns on and off VBUS power supply.
- 4.Customers can determine to use USB or UART communication according to their needs.

Application	Installed	Not installed
USB	R801~R804, Q801~Q802	U401 circuit
UART	U401 circuit	R801~R804, Q801~Q802

5.Please pay attention to GPS\_LNA\_EN voltage level translation for GPS LNA if MCU's GPIO is 5V voltage domain.

Quectel Wireless Solutions

DRAWN BY <Mountain.ZHOU>	PROJECT <UC20&M10 Reference Design>	TITLE <MCU Interface>
CHECKED BY <Bruce.YU>	SIZE A2	VER 1.01
SHEET 8 of 8		<2013.04>